

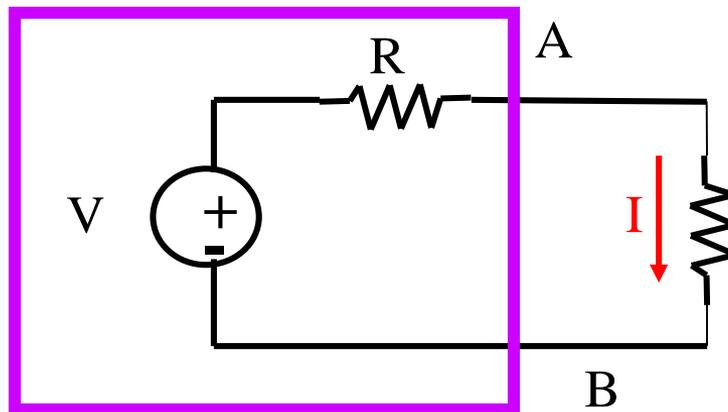
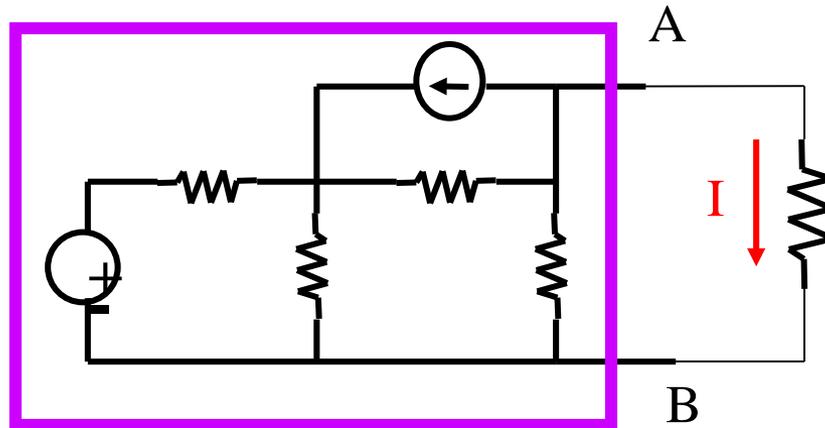


Thevenin's theorem

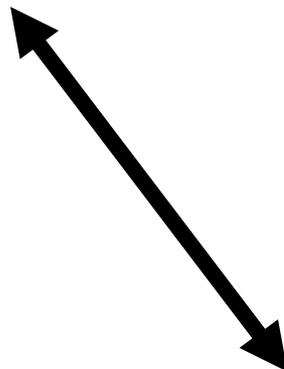



Thevenin's theorem

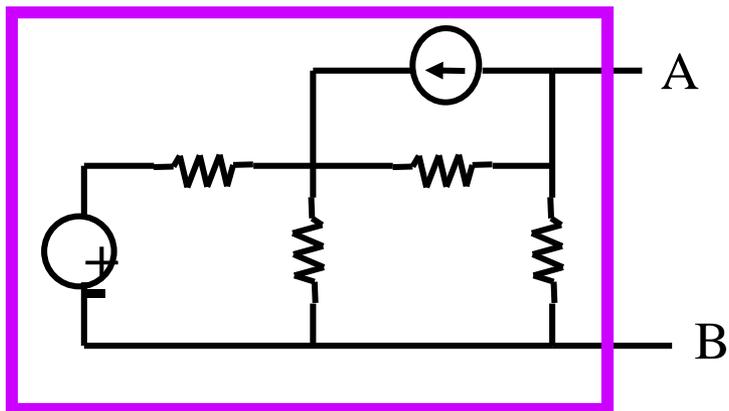

$$R_t = ?$$

$$V_{oc} = ?$$

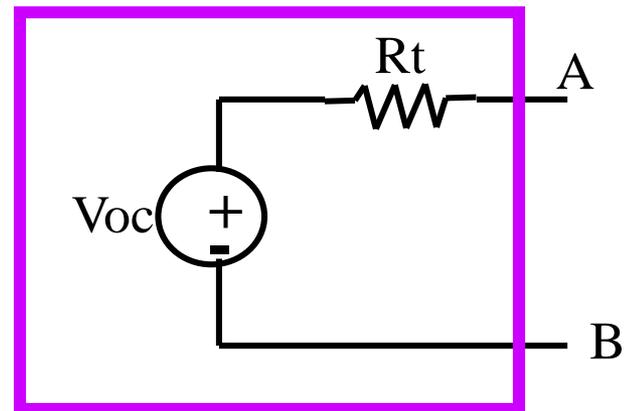

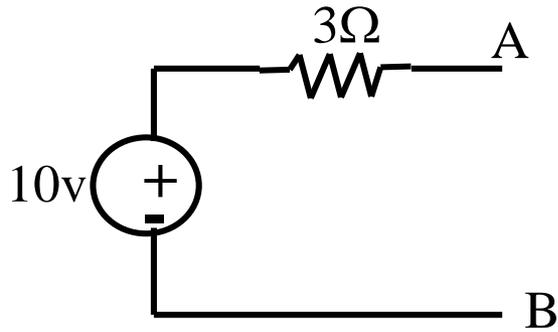


+
 V_{AB}
-

$$V_{AB} = ?$$

10v

apply KVL to get V_{AB}

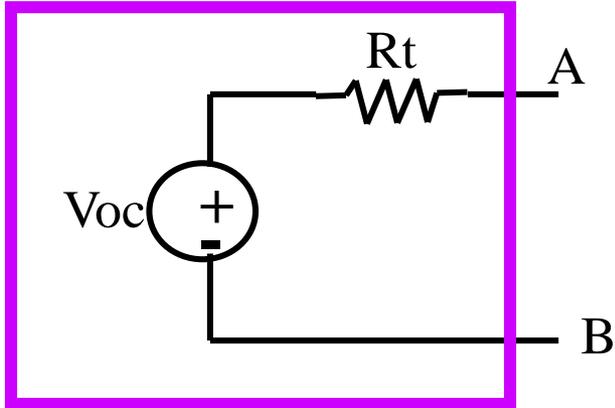


+
 V_{OC}
-

$$V_{AB} = V_{oc}$$

V_{oc} (Open Circuit)

V_{OC}


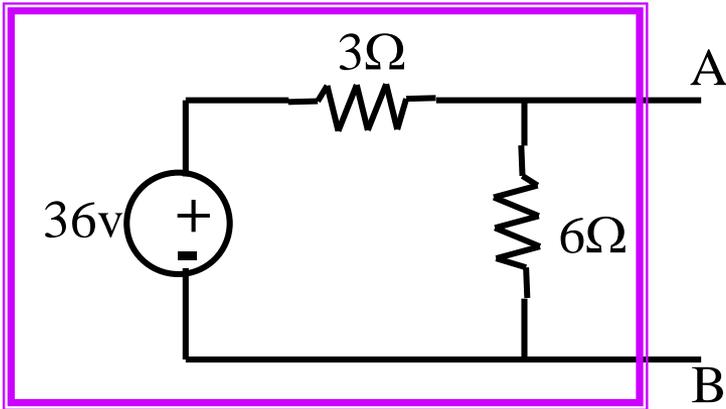


+
V_{OC}
-

V_{OC} = ?

V_{OC} (Open Circuit)

$$V_{OC} = \frac{6}{3 + 6} * 36 = 24$$

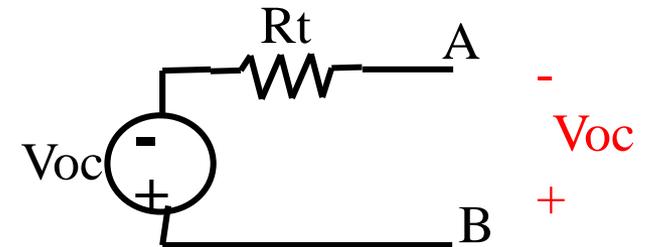
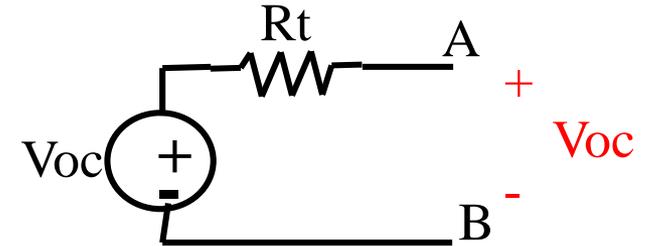


R_t

Method 1

• current source **OPEN CIRCUIT**


• voltage source **SHORT CIRCUIT**

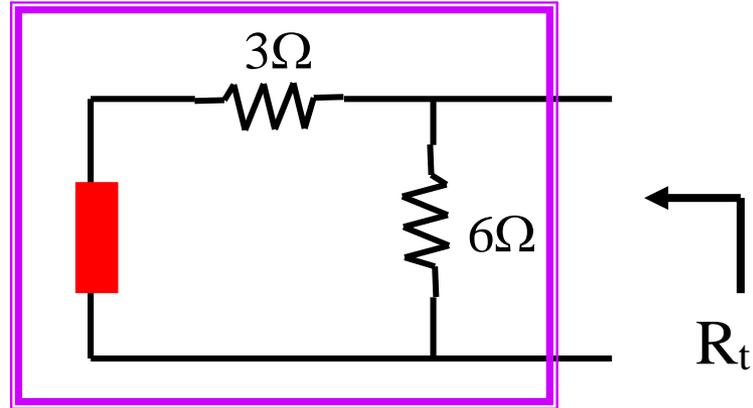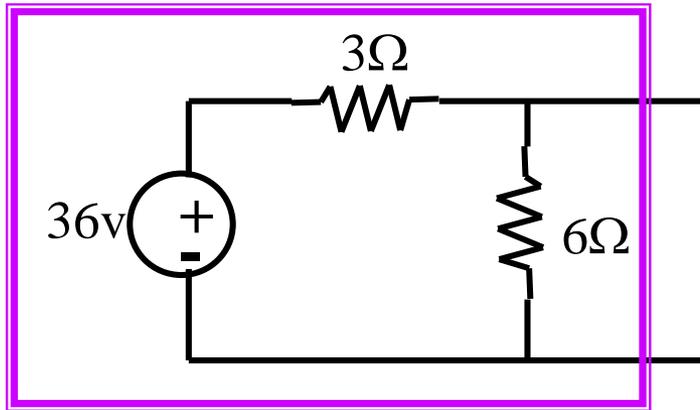

$$R_t = \frac{1}{\frac{1}{3} + \frac{1}{6}} = 2\Omega$$

R_t

Method 2

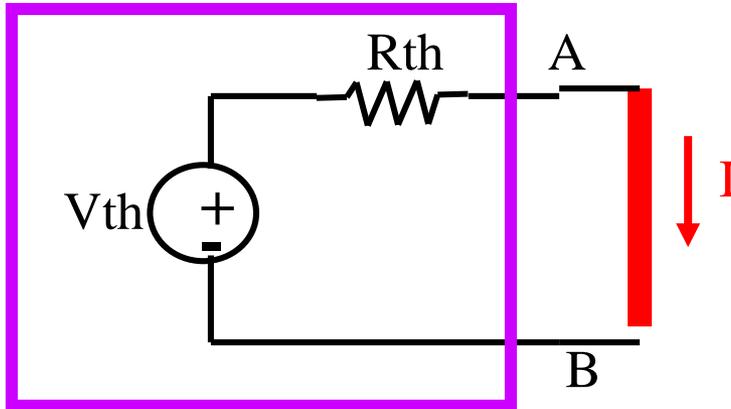

$I = I_{SC}$
(Short Circuit Current)






$$R_t = \frac{V_{oc}}{I}$$

$$R_t = \frac{V_{oc}}{I_{SC}}$$

R_t

Use Method 1

$R_t = ?$

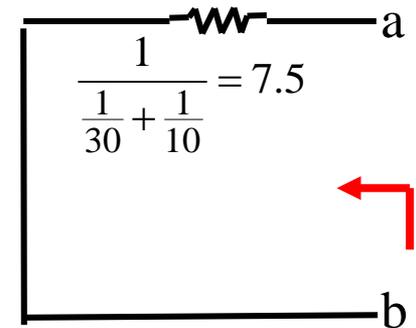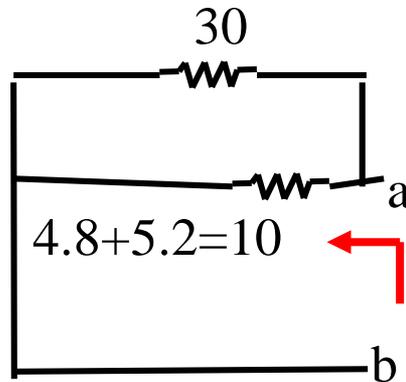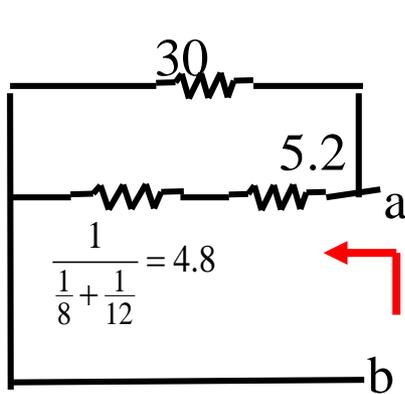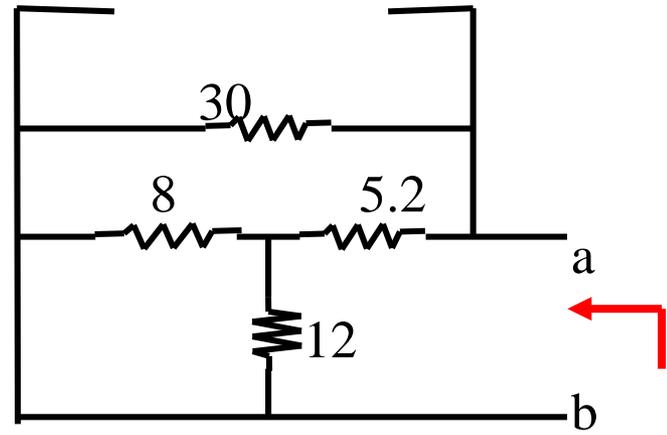
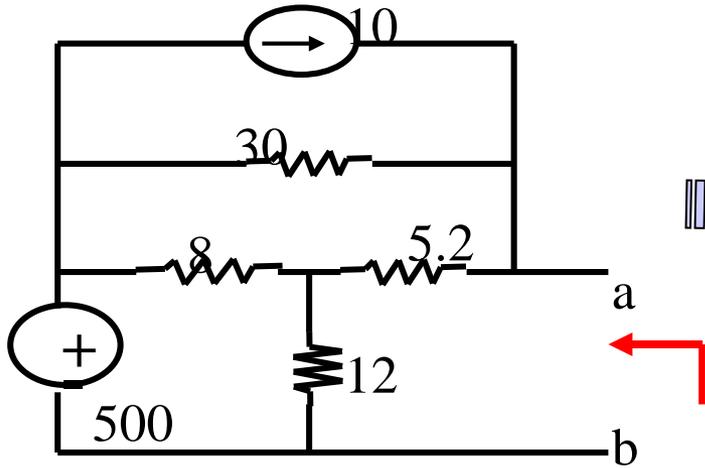


$R_t = 7.5\Omega$

R_t

Method 2


$$R_t = \frac{V_{oc}}{I_{sc}}$$

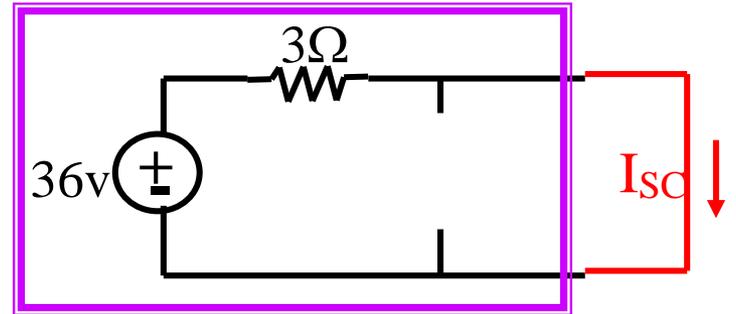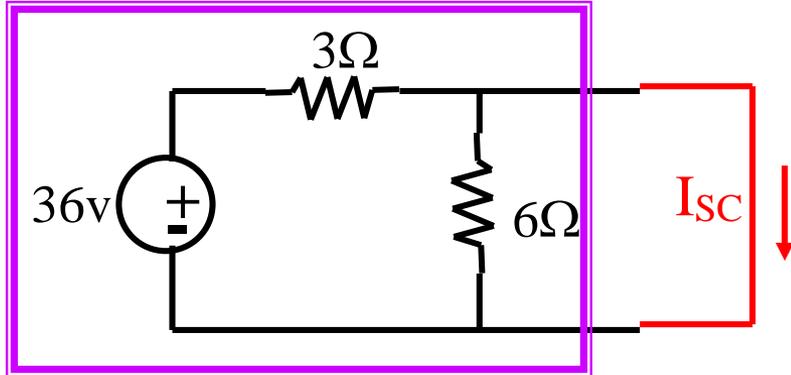

$$I_{sc} = \frac{36}{3} = 12A$$

$$R_t = \frac{V_{oc}}{I_{sc}} = \frac{24}{12} = 2\Omega$$


Norton's theorem

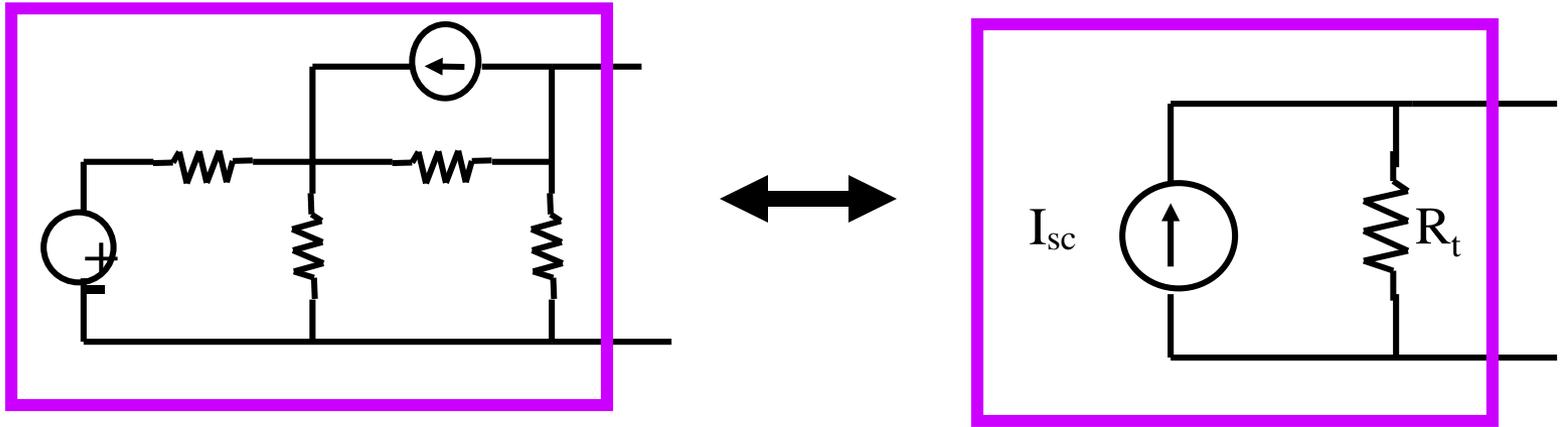

$$R_t = ?$$


$$I_{sc} = ?$$

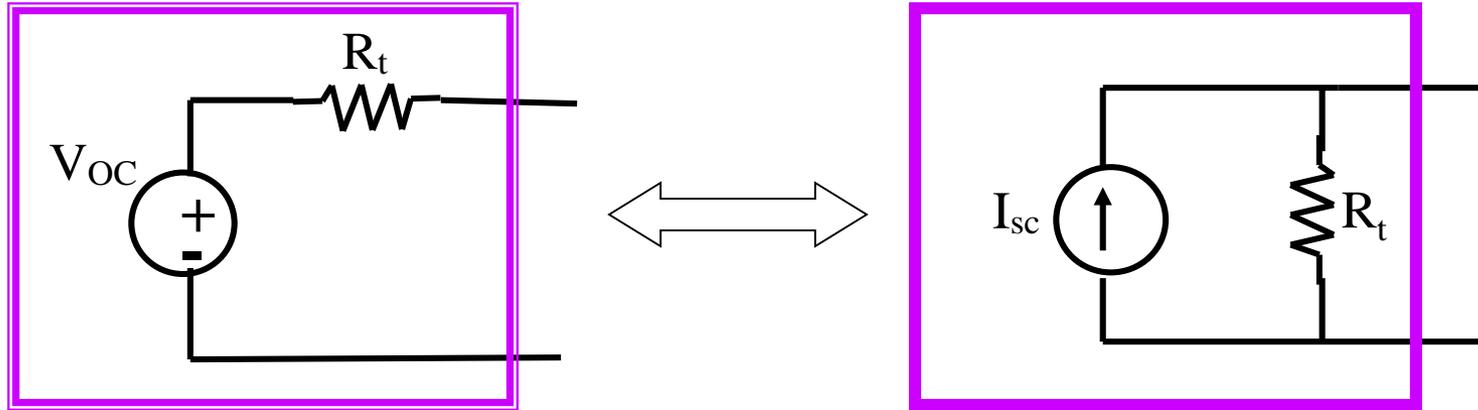Thevenin \Leftrightarrow Norton (Source Transform)




$$V_{oc} = I_{sc} R_t$$

$$I_{sc} = \frac{V_{oc}}{R_t}$$

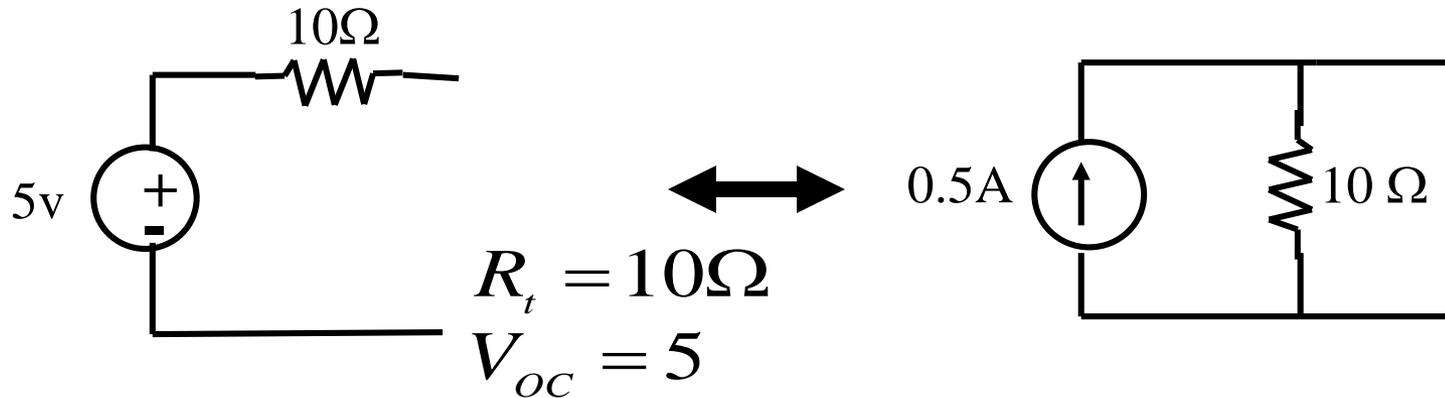


Ex.

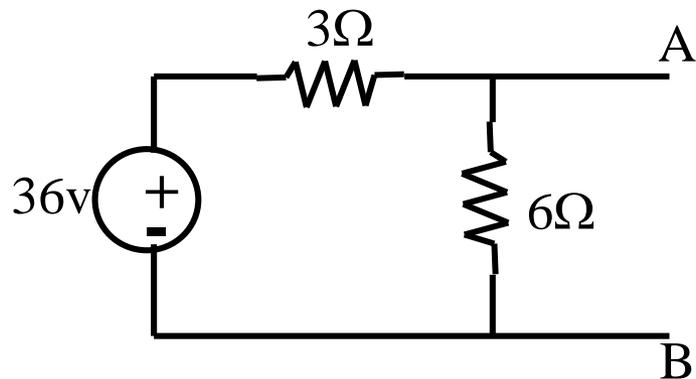

Thevenin equivalent at terminals A and B = ?


$$R_t = 2\Omega$$

$$V_{oc} = 24$$



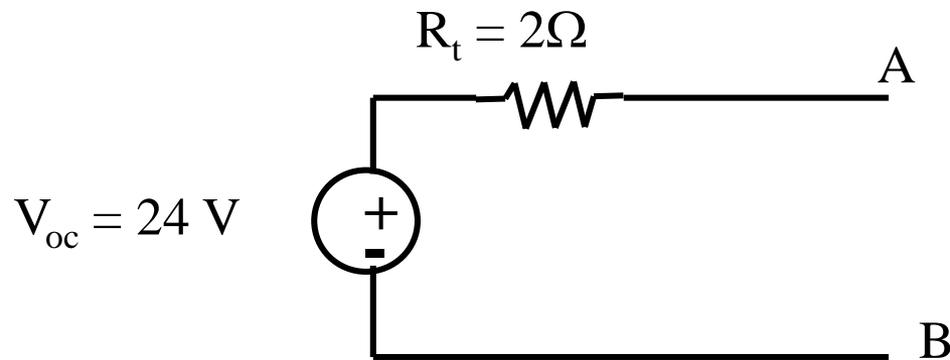


Ex.




By Thevenin's theorem

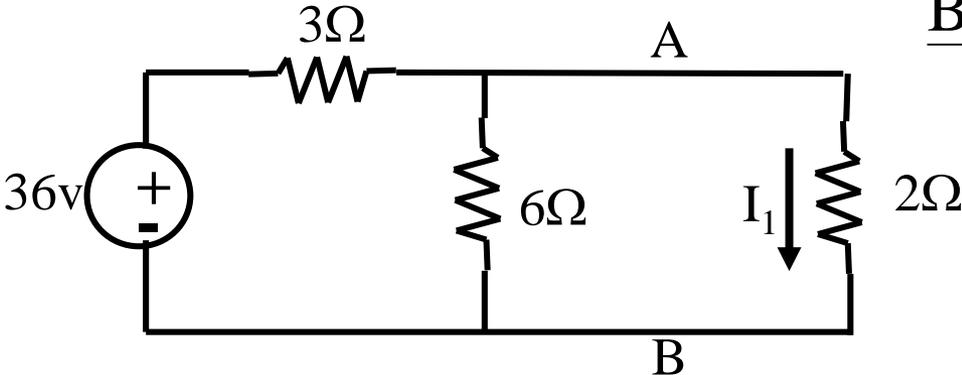

$I_1 = ?$

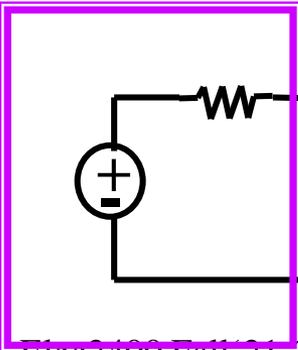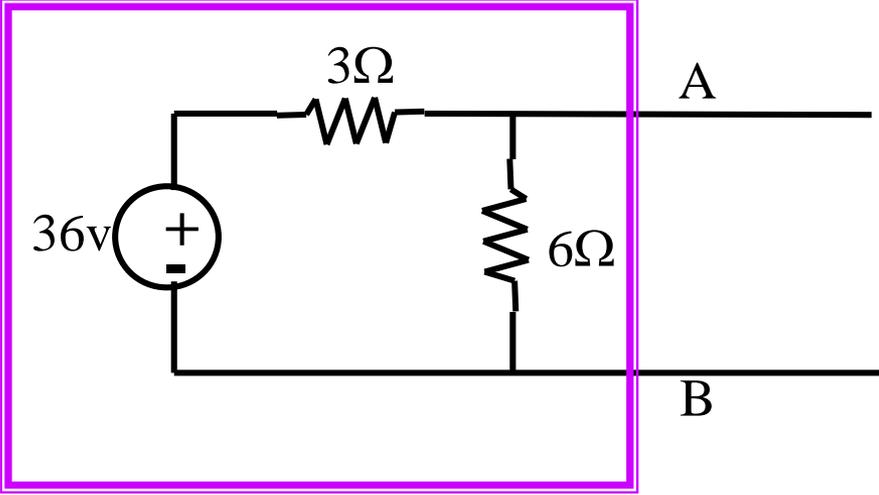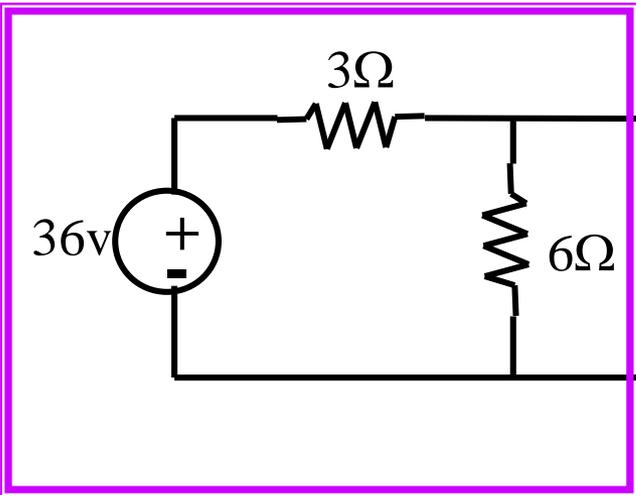


Ex.

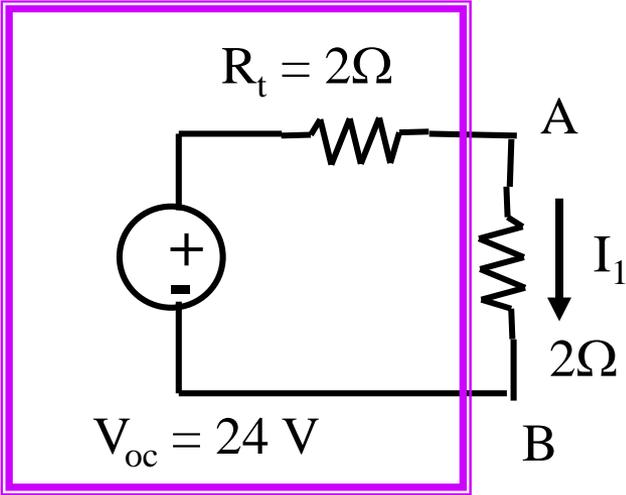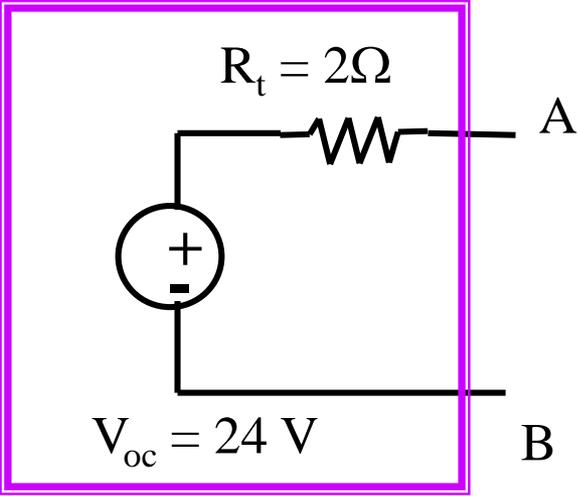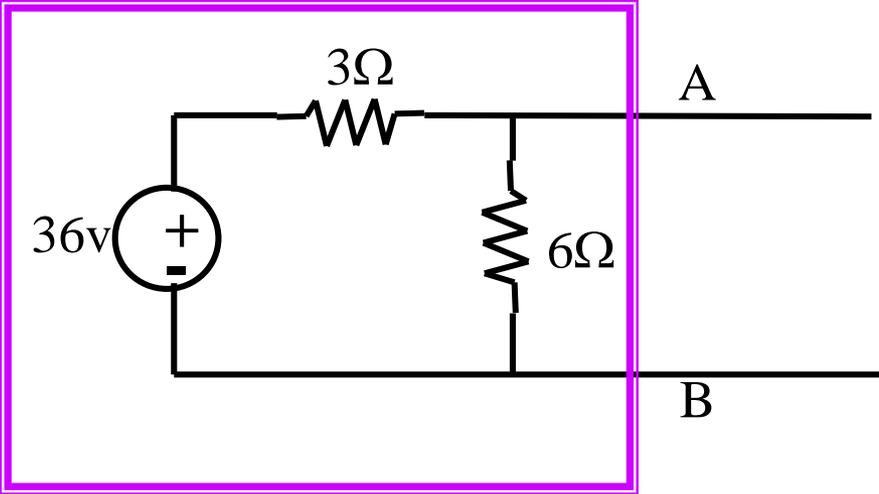




$$\begin{aligned}\Sigma \mathbf{V} &= 0 \\ 24 - 2\mathbf{I}_1 - 2\mathbf{I}_1 &= 0 \\ \mathbf{I}_1 &= 6 \text{ A}\end{aligned}$$

Ex.




By Norton's theorem

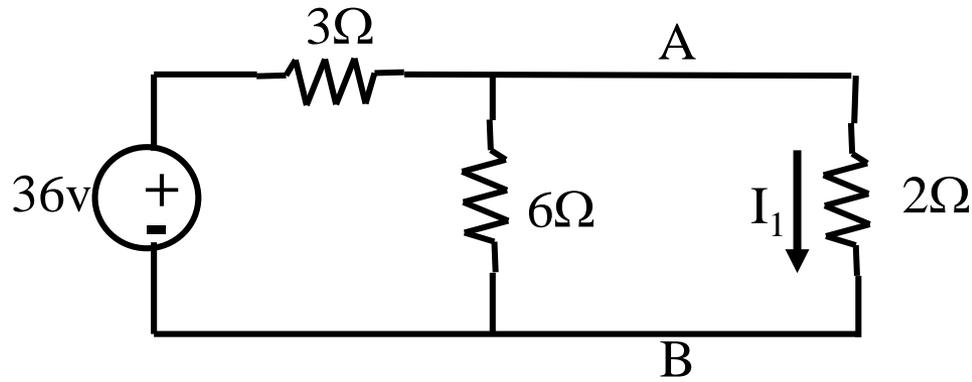

$$I_1 = ?$$

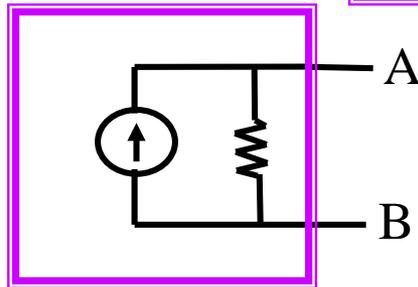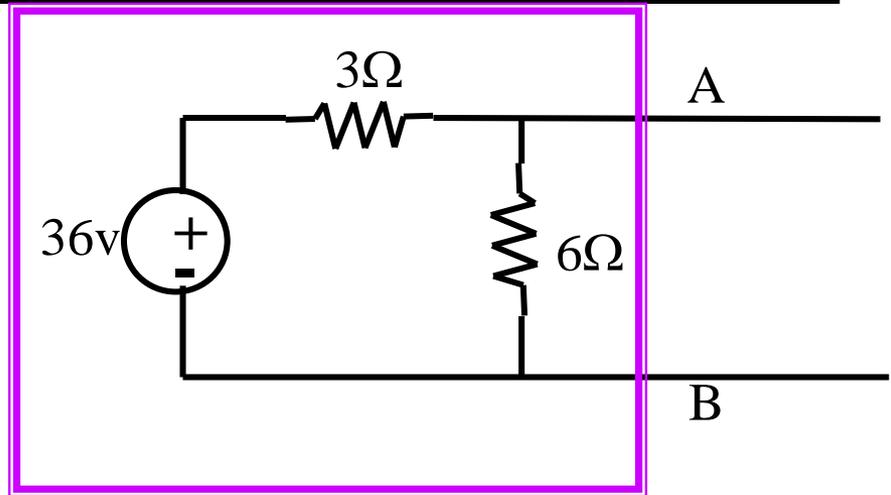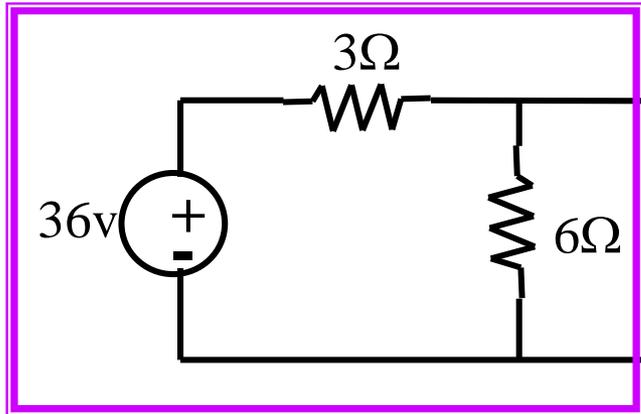

Ex.

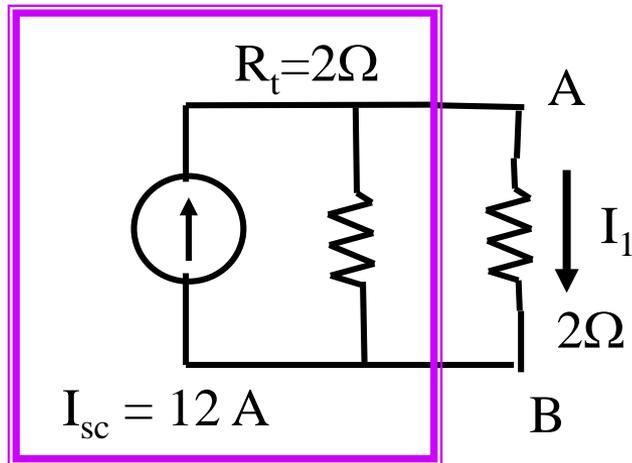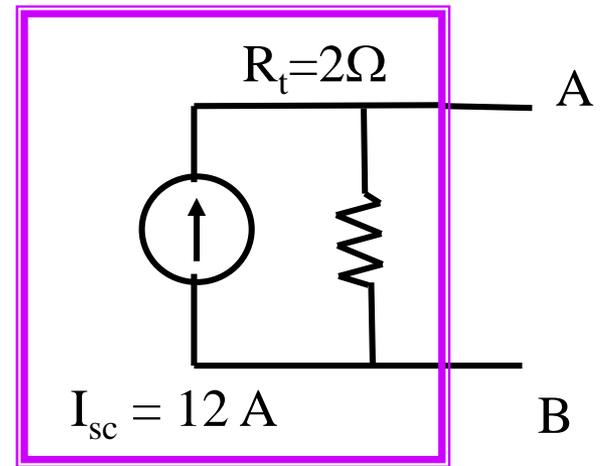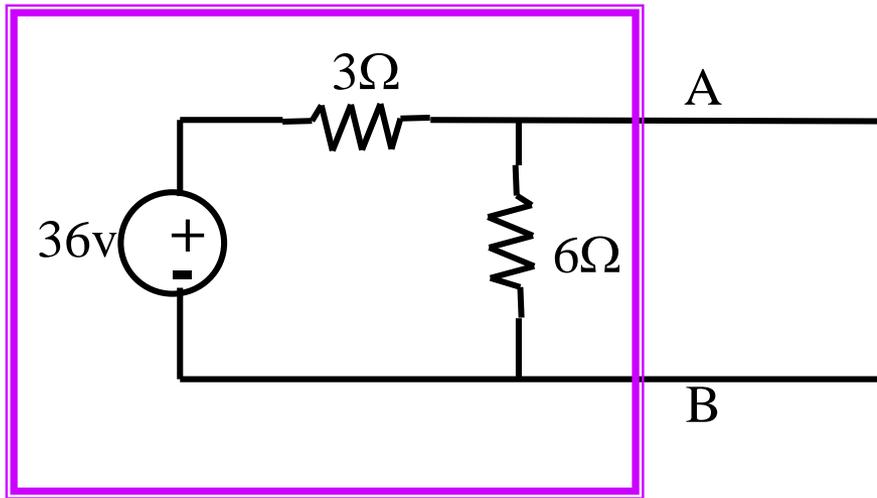

$$I_1 = \left(\frac{2}{2 + 2} \right) 12$$

$$I_1 = 6 \text{ A}$$